

Solution: Drawing the equivalent circuit,

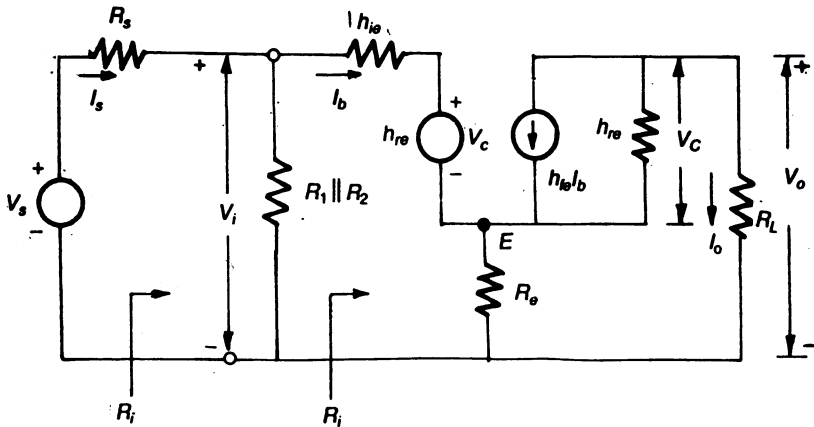


Fig. P. 5.15 (a)

From the circuit, we have,

$$-I_o = h_{fe}I_b + h_{oe}V_c \quad \dots(i)$$

$$V_c = V_o - (I_b - I_o) R_e = V_o - (I_b - I_o) \times 10^3 \dots(ii)$$

and, $V_o = + I_o R_L \quad \dots(iii)$

Substituting equations (ii) and (iii) in eq (i), we get

$$\begin{aligned} -I_o &= 50 I_b + 25 \times 10^{-6} (0.5 \times 10^3 \times I_o - 10^3 I_b + 10^3 I_o) \\ &= 49.75 I_b + 0.15 I_o \end{aligned}$$

or, $I_o = -43.3 I_b \quad \dots(iv)$

Also, $V_i = h_{ie}I_b + h_{re}V_c + (I_b - I_o) R_e \quad \dots(v)$

From eq. (ii)

$$\begin{aligned} V_c &= I_o R_L - (I_b - I_o) \times 10^3 \\ &= -43.3 \times 5 \times 10^3 I_b + 44.3 \times 10^3 I_b \end{aligned}$$

then from eq. (v),

$$\begin{aligned} V_i &= 1.1 \times 10^3 I_b + 2.5 \times 10^{-4} (-26.1 \times 10^4 I_b) + 44.3 \times 10^3 I_b \\ &= 45.3 \times 10^3 I_b \end{aligned}$$

Or, $R'_i = \frac{V_i}{I_b} = 45.3 \text{ K}$

then, $R_i = R'_i \parallel (9.1 \text{ K}) = \frac{45.3 \text{ K} \times 9.1 \text{ K}}{54.4 \text{ K}} = 7.58 \text{ K}$

Problem 5.18:

(a) For the two-transistor amplifier circuit shown (supply voltages are not indicated) calculate A_I , A_v , A_{v_s} , and R_i . The

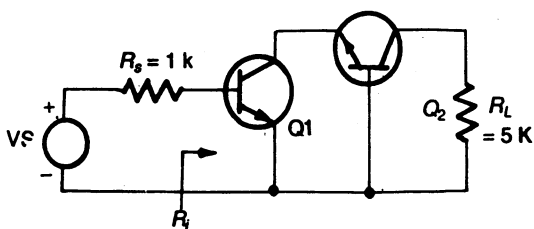


Fig. P. 5.18

transistors are identical, and their parameters are given in Table 5.1.

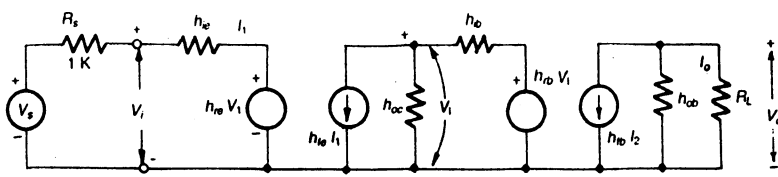
Solution:

Fig. P. 5.18 (a)

From the circuit,

$$V_i = h_{ie}I_1 + h_{re}V_1 \quad \dots(i)$$

$$V_1 = h_{ib}I_2 + h_{rb}V_o \quad \dots(ii)$$

$$V_o = -I_o R_L = -h_{fb}I_2 R_L \left[\because \frac{1}{h_{ob}} \gg R_L \right] \quad \dots(iii)$$

$$\text{and, } I_2 = -h_{oe}V_1 - h_{fe}I_1 \quad \dots(iv)$$

Substituting equation (ii) and (iii) in eq. (iv), we have

$$\begin{aligned} I_2 &= -h_{fe}I_1 - h_{oe}(h_{ib}I_2 + h_{rb}V_o) \\ I_2 &= -h_{fe}I_1 - h_{oe}(h_{ib}I_2 - I_o R_L h_{rb}) \\ &= -50 I_1 - h_{oe}[h_{ib}I_2 - h_{fb}I_2 R_L h_{rb}] \end{aligned}$$

$$\text{Putting, } h_{oe} = 24 \times 10^{-6} \mu\text{A/V}$$

$$h_{ib} = 21.6 \Omega$$

$$h_{fb} = -0.98$$

$$h_{rb} = 2.9 \times 10^{-4}$$

$$R_L = 5\text{K}$$

$$h_{ie} = 1.1\text{K}$$

and, $V_1 = h_{ie} I_1$

or, $R_{i_2} = \frac{V_1}{I_1} = h_{ie}$

and, voltage gain for stage II

$$A_{V_2} = \frac{A_{I_2} \times R_L}{R_{i_2}} = \frac{-50 \times 0.7}{1.1} = -31.9$$

Now, $\gamma_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ice} + R_s} = 0$

then, $R_{o_2} = \frac{1}{\gamma_o} = \infty$

Stage I: In this stage, circuit drawn is shown below.

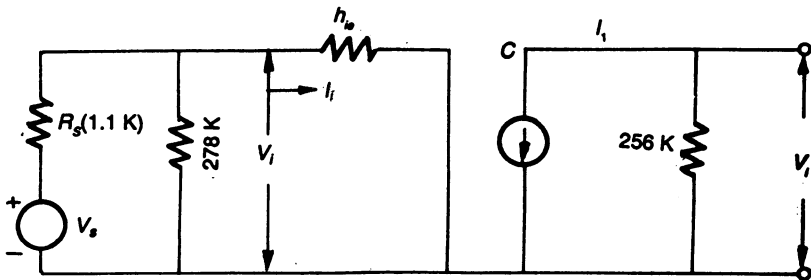


Fig. P. 5.21 (b)

Since $h_{oc} R_L = h_{oe} [R_{c_1} \parallel (R_{i_2} \parallel R_{22}) \parallel R_{i_2}]$

$$= \frac{1}{40} \times [6 \text{ K} \parallel 4.46 \text{ K} \parallel 1.1 \text{ K}] = 0.02 \leq 0.1$$

So, we can use appropriate analysis for this stage also.

Now drawing the equivalent circuit

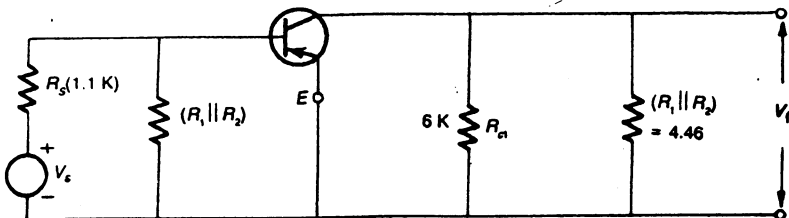
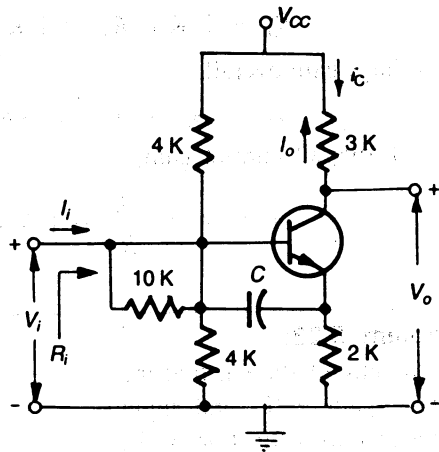


Fig. P. 5.21 (d)

Problem 5.24:

For the bootstrap circuit shown, calculate $A_I \equiv I_o/I_i$, R_i and A_v . The transistor parameters are $h_{ie} = 2 \text{ K}$, $h_{fe} = 100$, $1/h_{oe} = 40 \text{ K}$, and $h_{re} = 2.5 \times 10^{-4}$.

**Fig. P. 5.24**

Solution: The Ckt. is viewed from emitter side, and the effective emitter resistance is,

$$R'_e = (2 \text{ K} \parallel 4 \text{ K} \parallel 4 \text{ K}) = 1 \text{ K}$$

Since,

$$h_{oe} (R_c + R'_e) = \frac{4}{40} = 0.1$$

Hence, we can use the approximate analysis for the convenience

$$\text{Thus, } A'_I = \frac{I_o}{I_b} = -h_{fe} = -100$$

$$\begin{aligned} R'_i &= \frac{V_i}{i_b} = h_{ie} + (1 + h_{fe}) R'_e \\ &= 2 \text{ K} + 101 \times 1 = 103 \text{ K} \end{aligned}$$

Now the voltage gain from base to emitter :

$$A'_v = \left(1 - \frac{h_{re}}{R_i} \right) = 1 - \frac{2}{103} = 0.9806$$

Now applying Miller's theorem to 10 K

$$\text{we find, } R_1 = \frac{10}{1 - 0.9806} = 515 \text{ K}$$