

1. Fundamentals of Electrical Engineering—Circuit Theory Concepts	1–34
1.1 Introduction 1	
1.1.1 Electric Charge and Electric Current 1	
1.1.2 Direction of Current 2	
1.1.3 Coulomb's Law 3	
1.2 Electromotive Force and Potential Difference 3	
1.3 Ohm's Laws 5	
1.4 Basic Parameters of Circuit (R–L–C) 6	
1.4.1 Resistance 6	
1.4.2 Inductance 9	
1.4.3 Capacitance 12	
1.4.4 Capacitance in Series 13	
1.4.5 Capacitors in Parallel 14	
1.4.6 Capacitance of a Parallel Plate Capacitor 14	
1.4.7 Capacitance of Concentric Spheres 15	
1.4.8 Capacitance of Two Coaxial Cylinders 16	
1.5 Electromagnetic Induction 17	
1.6 Laws of Electromagnetic Induction 17	
1.7 Kirchhoff's Laws 18	
1.8 Ampere's Law 19	
1.9 Sources 20	
1.9.1 Source Transformation 21	
2. Electrical Circuit Analysis	35–94
2.1 Circuit Concepts 35	
2.1.1 Concept of Network/Circuit 35	
2.2 Network Terminology 35	
2.3 Classification of Electrical Networks 37	
2.4 Basic Circuit Elements 38	
2.5 Energy Sources 39	
2.6 Current Division Rule 41	
2.7 Voltage Division Rule 41	
2.8 Source Transformation 41	
2.8.1 Transformation of Voltage Source to Current Source 42	
2.8.2 Transformation of Current Source to Voltage Source 42	

- 2.9 Kirchhoff's Law's 46
 - 2.9.1 Kirchhoff's Current Law (KCL) or First Law 46
 - 2.9.2 Kirchhoff's Voltage Law (KVL) or Second Law 47
- 2.10 Loop Analysis or Mesh Analysis 47
- 2.11 Nodal Analysis 49
- 2.12 Star-delta Transformation 51
 - 2.12.1 Network Reduction By Delta-Star and Star-Delta Transformation 52

3. AC Fundamentals

95–127

- 3.1 Introduction 95
 - 3.1.1 AC Quantity 95
- 3.2 Types of AC Waveforms 95
- 3.3 Advantages of Sinusoidal Waveforms 96
- 3.4 Generation of Alternating Quantity 96
 - 3.4.1 Equations of the Alternating Voltages and Currents 97
- 3.5 Important Definitions Related to AC Quantity 98
- 3.6 Important Values of Alternating Quantities 101
- 3.7 Root Mean Square (RMS) or Effective Values, Average Value, Form-Factor and Peak Factor of Alternating Current and Alternating Voltage for Sinusoidal Waveform 101
- 3.8 RMS Value or Effective Value, Form Factor for Half-wave Voltage and Current 104
- 3.9 RMS Value, Average Value, Form Factor and Peak Factor for Square Wave of Voltage and Current 105
- 3.10 RMS Value, Average Value, Form Factor, Peak Factor of Triangular Wave for Current and Voltage 106
- 3.11 Concept of Phasor 109
 - 3.11.1 Phasor Diagram Using RMS Values 110
 - 3.11.2 Phase and Phase Angle 110
 - 3.11.3 Phase Difference 110
 - 3.11.4 Conventions for Drawing Phasor Diagrams 112
- 3.12 Addition and Subtraction of Alternating Quantities 113

4. Steady State Analysis of Single Phase AC Circuits

128–194

- 4.1 Introduction 128
- 4.2 AC Circuit 128
 - 4.2.1 AC Circuit Containing Pure Resistor Only 128
 - 4.2.2 AC Circuit Containing Pure Inductor Only 131
 - 4.2.3 AC Circuit Containing Pure Capacitance Only 133
- 4.3 AC Series Circuit 136
 - 4.3.1 AC Circuit Containing Resistance and Inductance in Series 136
 - 4.3.2 Apparent Power, Real Power and Reactive Power 139
 - 4.3.3 AC Circuit Containing Resistance and Capacitance in Series 140
- 4.4 AC Circuit Containing Resistance, Inductance and Capacitance in Series (R-L-C Series) 144
 - 4.4.1 Impedance Triangle 145
 - 4.4.2 Power and Power Triangle 146
- 4.5 AC Parallel Circuit 147
- 4.6 Method of Solving AC Parallel Circuit 148
 - 4.6.1 By Phasor Diagram Method 148
 - 4.6.2 By Phasor Algebra 149

- 4.6.3 Impedance Method 150
- 4.6.4 Admittance Method 151
- 4.7 Resonance in R-L-C Circuits 154
 - 4.7.1 Introduction 154
 - 4.7.2 Series or Voltage Resonance 155
 - 4.7.3 Graphical Representation of Resonance in An R-L-C Series Circuits 156
 - 4.7.4 Resonance Curve 156
 - 4.7.5 Determination of Bandwidth and Edge Frequencies 157
 - 4.7.6 Quality Factor of a Series Resonant Circuit 158
 - 4.7.7 Parallel or Current Resonance 159
 - 4.7.8 Q-factor or Current Magnification Factor for Parallel Resonance Circuit 161

5. DC Network Theorems

195–272

- 5.1 Introduction 195
- 5.2 Superposition Theorem 195
 - 5.2.1 Steps to Solve Problems on Superposition Theorem 195
- 5.3 Thevenin's Theorem 199
 - 5.3.1 Steps for Solving Problems 200
 - 5.3.2 Applications 201
 - 5.3.3 Advantages 201
 - 5.3.4 Disadvantages 201
- 5.4 Norton's Theorem 207
 - 5.4.1 Steps for Solving Problems on Norton's Theorem 207
- 5.5 Maximum Power Transfer Theorem 211
 - 5.5.1 Proof of Maximum Power Transfer Theorem 211
 - 5.5.2 Steps for Solving Problems on Maximum Power Transfer Theorems 212
- 5.6 Reciprocity Theorem 212

6. AC Network Theorems

273–316

- 6.1 Introduction 273
- 6.2 Star–Delta and Delta–Star Transformations 273
 - 6.2.1 Delta to Star Conversion 274
 - 6.2.2 Star to Delta Conversion 275
- 6.3 Source Transformations 275
- 6.4 Network Terminology 277
 - 6.4.1 Loop and Mesh 277
 - 6.4.2 Node and Junction 277
 - 6.4.3 Sign Convension 277
- 6.5 Kirchhoff's Laws 277
 - 6.5.1 Super-Node Analysis 278
 - 6.5.2 Super-Mesh Analysis 279
- 6.6 Superposition Theorem 280
 - 6.6.1 Applications of Superposition Theorem 280
 - 6.6.2 Limitations of Superposition Theorem 280
- 6.7 Thevenin's and Norton's Theorems 280
 - 6.7.1 Procedure to Obtain V_{th} and Z_{th} or I_N and Z_n 281
 - 6.7.2 Applications of Thevenin's and Norton's Theorems 282
 - 6.7.3 Limitations 282
 - 6.7.4 Application of Millman's Theorem 285
 - 6.7.5 Limitations of Milliman's Theorem 285
- 6.8 Maximum Power Transfer Theorem 285

7. Three Phase AC Circuit	317–341
7.1 Introduction	317
7.2 Three Phase Electric System	317
7.2.1 Comparison of Single Phase and Three Phase Systems	318
7.3 Balanced or Unbalanced Load	318
7.4 Generation of 3- ϕ EMFs	319
7.5 Phase Voltage, Phase Current, Line Voltage and Line Current	319
7.6 Star (Y) Connected System	320
7.6.1 Power in 3- ϕ AC System	320
7.7 Delta (Δ) Connection System	321
7.8 Measurement of Power in 3- ϕ AC Circuit	322
7.8.1 One Wattmeter Method	322
7.8.2 Two Wattmeter Method	322
7.8.3 Three Wattmeter Method	326
8. Transients	342–358
8.1 Introduction	342
8.2 Types of Transients	342
8.3 Important Differential Equations	343
8.4 Transients in R-L Circuit (DC)	344
8.5 Short Circuit Current	346
8.6 Time Constant	347
8.7 Transients in R-L Circuits (AC)	347
8.8 Transients in R-C Series Circuits (DC)	349
8.9 Transients in R-C Series Circuits (AC)	351
8.10 Double Energy Transients	352
9. Measuring Instruments	359–371
9.1 Introduction	359
9.2 Classification	359
9.3 Operation of Indicating Instruments	360
9.4 Types of Measuring Instruments	360
9.4.1 Permanent Magnet Moving Coil Instrument (PMMC)	361
9.4.2 Dynamometer Type Instrument	363
9.4.3 Dynamometer Type Wattmeter	363
9.5 Extension of Range of Moving Coil Instrument	365
9.6 Moving Iron Instrument	367
10. Magnetic Circuits	372–392
10.1 Introduction	372
10.2 Magnetic Circuit Concept	372
10.3 Magnetic Circuit with DC Excitations	375
10.4 Analogy between Electric and Magnetic Circuits	377
10.5 Magnetic Circuit Calculation	379
10.6 Electromagnetism	379
10.7 Nature of Induced EMF	380
10.7.1 Magnetic Leakage and Fringing	381
11. Single Phase Transformer	393–430
11.1 Introduction	393
11.2 Transformer as a Device	393

- 11.3 Classification of Transformer 394
- 11.4 Principle of Operation of Transformer 395
- 11.5 EMF Equation of Transformer 396
- 11.6 Transformation Ratio (K) 397
- 11.7 Ideal Transformer 398
- 11.8 Practical Transformer 398
- 11.9 Practical Transformer on No-Load 399
- 11.10 Transformer on Load 399
- 11.11 Equivalent Circuit Diagram 402
- 11.12 Losses in Transformer 405
- 11.13 Transformer Efficiency 407
 - 11.13.1 Condition for Maximum Power Efficiency 408
 - 11.13.2 Voltage Regulation of a Transformer 408
 - 11.13.3 Efficiency from Transformer Tests 410
 - 11.13.4 Calculation of Efficiency from OC and SC Test 411
- 11.14 Auto Transformer 412

12. DC Machines

431–460

- 12.1 Introduction 431
- 12.2 Concept of Electro-Mechanical Energy Conversion 431
- 12.3 Types of DC Machines 431
 - 12.3.1 Separately Excited DC Machine 432
 - 12.3.2 Self Excited DC Machine 432
- 12.4 Construction of DC Machine 434
 - 12.4.1 Yoke 435
 - 12.4.2 Pole Core and Pole Shoes 435
 - 12.4.3 Field Coils 435
 - 12.4.4 Armature Core 436
 - 12.4.5 Armature Winding 437
 - 12.4.6 Commutator 437
 - 12.4.7 Brush Assembly and Brush Gear 437
 - 12.4.8 Bearings 437
- 12.5 Working of DC Generator 437
- 12.6 EMF Equation of DC Generator 439
- 12.7 Important Relations for Various Types of DC Generators 441
 - 12.7.1 Separately Excited DC Generator 441
 - 12.7.2 Shunt Wound DC Generator 442
 - 12.7.3 Series Wound DC Generator 442
 - 12.7.4 Compound Wound DC Generator 443
- 12.8 Working Principle of DC Motor 446
 - 12.8.1 Significance of Back EMF in DC Motor 446
 - 12.8.2 Important Relations for Different Types of DC Motors 447
- 12.9 Torque Developed in a Motor 451
- 12.10 Characteristics of DC Motors 453
 - 12.10.1 Characteristics of DC Shunt Motor 453
 - 12.10.2 Characteristics of DC Series Motor 454
 - 12.10.3 Characteristics of DC Compound Motors 455

13. Induction Motors	461–483
13.1 Three Phase Induction Motor	461
13.2 Construction of 3- ϕ Induction Motor	462
13.3 Operation of 3- ϕ Induction Motor	462
13.4 Slip Speed, Slip, Synchronous Speed	463
13.4.1 Rotor Frequency (f_r)	463
13.4.2 Rotor Current, Rotor Power Factor	463
13.5 Power Stages in 3- ϕ Induction Motor	464
13.6 Electromagnetic Torque Expression for 3- ϕ Induction Motor	465
13.7 Torque Slip and Torque-Speed Characteristics of 3- ϕ Induction Motor	465
13.8 Need of a Starter for 3- ϕ Induction Motor and Starting Method of 3- ϕ Induction Motor	466
13.8.1 DOL (Direct Online Starter)	467
13.8.2 Reduced Voltage Starting	467
13.8.3 Auto-Transformer Starting	468
13.8.4 Star-Delta Method of Starting	468
13.9 Some Important Formulae	469
13.10 Single Phase Induction Motor	476
13.11 Construction of a Single Phase Induction Motor	476
13.12 Working Principle of Single Phase Induction Motor	476
13.13 Why Single Phase Induction Motor is not Self-Starting	477
13.13.1 Double Revolving Field Theory	477
13.13.2 Single Phase Induction Motor is Self-Starting	478
13.14 Types of Single Phase Induction Motor or Phase Splitting Method of Starting	478
13.14.1 Split Phase Induction Motor	479
13.14.2 Capacitor Start Induction Motor	480
13.14.3 Capacitor Start Capacitor Run Motor	480
13.14.4 Shaded Pole Motor	482
14. Three Phase Synchronous Machines	484–490
14.1 Introduction	484
14.2 Construction of an Alternator	484
14.3 Principle of Operation of an Alternator	485
14.4 Frequency of Induced EMF	486
14.5 Synchronous Motor	487
14.6 Operating Principle	487
14.7 Method of Starting a Synchronous Motor	489
14.8 V-Curves	489
14.9 Application of Three Phase Synchronous Motor	489
14.10 Disadvantages of Synchronous Motors	489
Index	491–492